

Experiment Name: Blinking LED using pic Microcontroller

Objective(s) :

- ① Designing a LED blinking circuit
- ② Understanding the circuit diagram of pic Microcontroller

Theory: LED's are small powerful lights that are used in many application. It is as simple as light turning on and off. LED is a electronic device, which has its terminals.

An LED is a two-terminal device. The two terminals are called as cathode and anode.

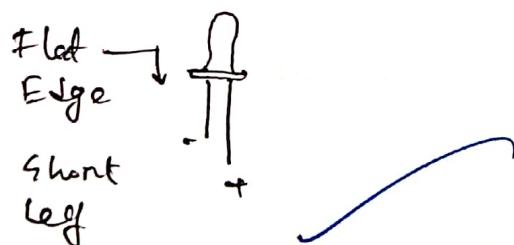


fig: a Structure of LED

Apparatus Required's:

LED, pic16F877A, power supply, resistor, crystal oscillator, capacitor.

circuit diagram:-

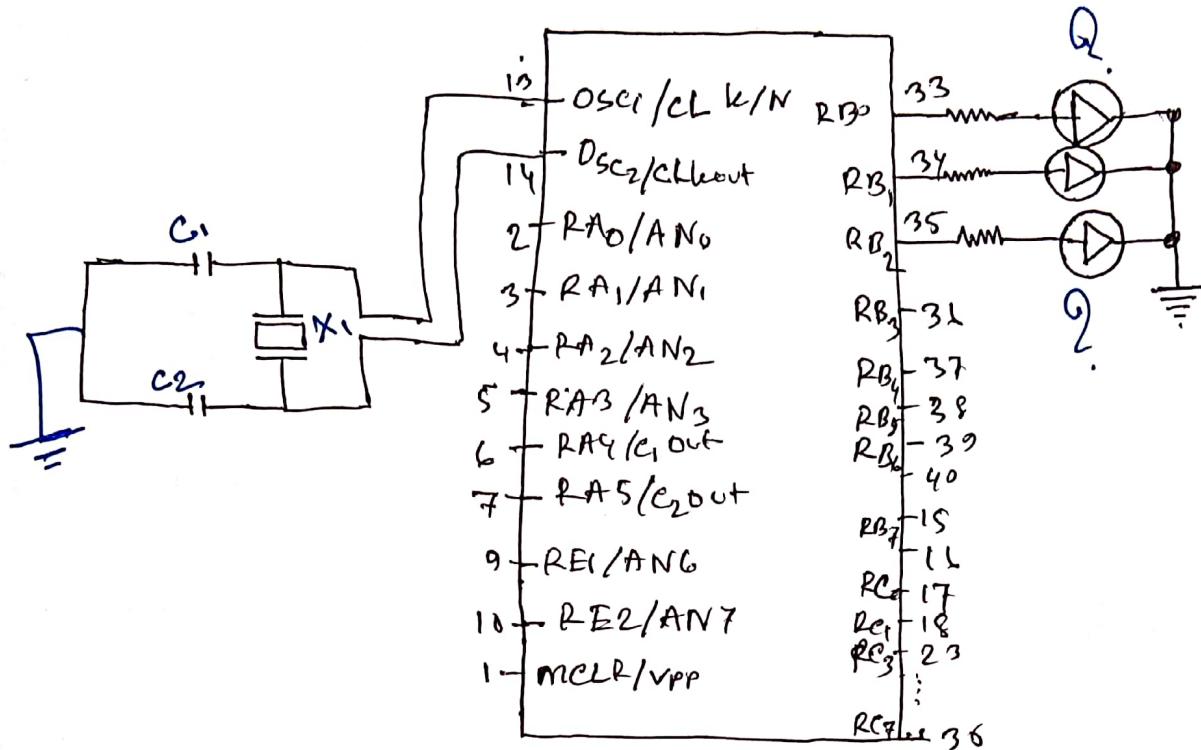


figure No: 1 PIC 16F877A

Program:

```
void main()
{
    TRISB = 0x00;
    PORTB = 0x00;

    while(1)
    {
        pnotb.f0 = 0xFF;
        delay.ms(400);
        pnotb.f0 = 0x11;
        pnotb.f1 = 0xFF;
        delay.ms(400);
        pnotb.f1 = 0x00;
        port.f2 = 0xFF;
        delay.ms(400);
    }
}
```

Name of Experiment: Write a program to count 0 to 9 in 7 segment display using PIC microcontroller.

Objectives:

- ① ~~Learning~~ to design a 7 segment display using PIC microcontroller
- ② ~~Understanding~~ ^{To understand} 7 segment display principal

Theory:

Seven segment displays are the output display device that provides a way to display information in the form of image or text on decimal numbers which is an alternative to the more complex dot matrix display. It is widely used in digital clock basic calculator, electronic meters and other electronics devices that displaying numerical information. It consists of seven segment of light-emitting diode which are assembled like numerical 8.

According to the type of application, there are two types of configuration of seven segment display.

- ① Common anode display.
- ② Common cathode display.

① In common cathode segment displays, all the cathode connection of led segment are connected together to logic or ground. We use logic 1 through a current limiting resistor to forward bias the individual anode terminal a to g.

② whereas the anode connections of the LED segment are connected together to logic in a common anode seven segment display. we use logic through a current limiting resistor to the cathode of a particular segment a to g



Common anode seven segment display are more popular than cathode seven segment display because logic circuit can sink more current than they can source and if it is the same as connecting LEDs is reverse.

Digital clocks, calculators, radios.

Apparatus required:-

pic 16F877A, capacitor, resistor, crystal, common anode 7 segment

Circuit diagram:-

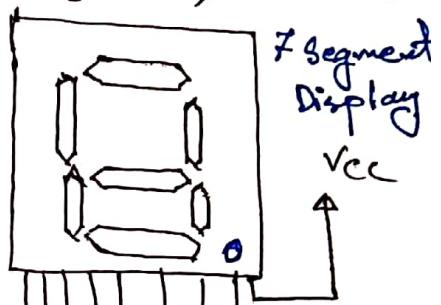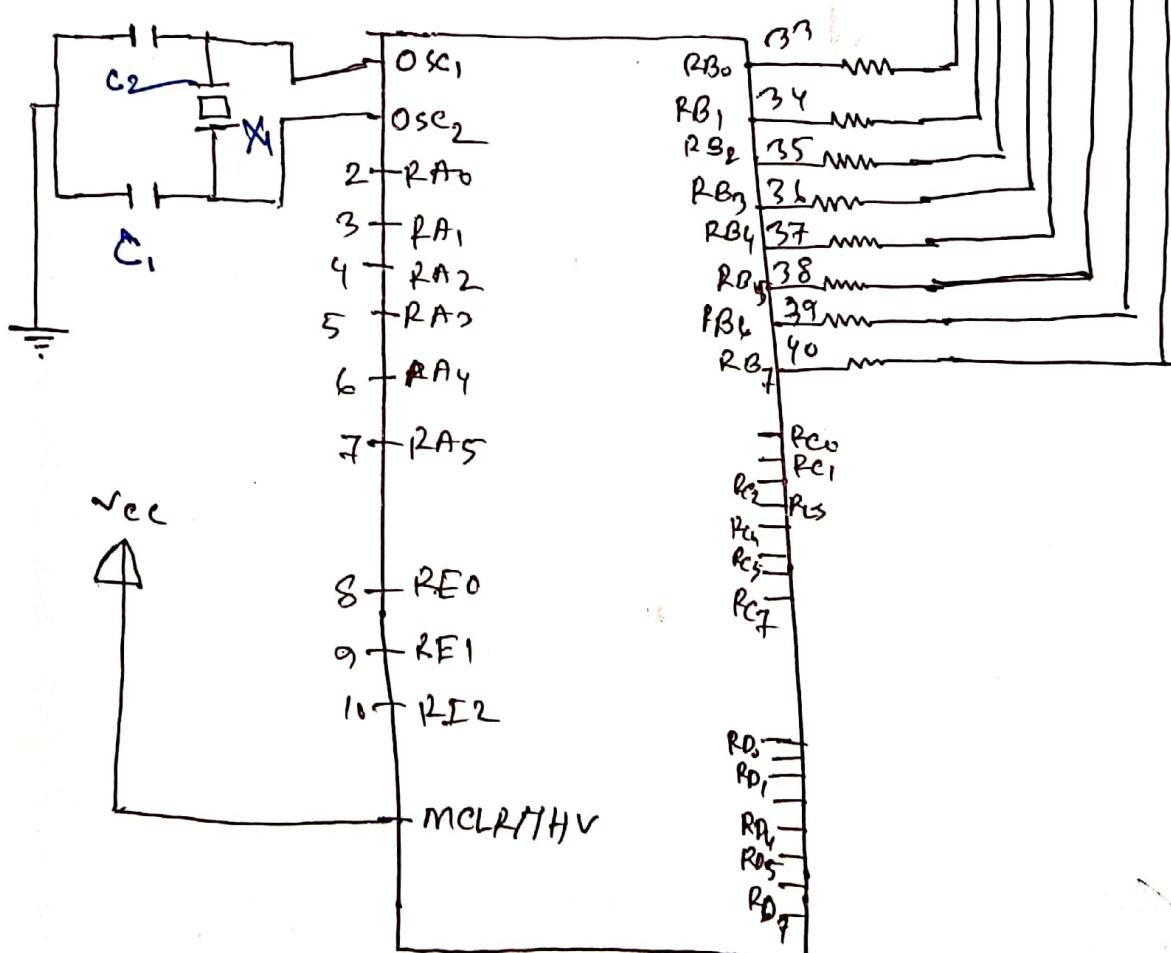

PIC 16F877A

figure Caption?

Code:

```
Void main()
{
    int i=0
    char arra[ ] = {0x90, 0x79, 0x24, 0x30,
                    0x19, 0x12, 0x02, 0x78}
    TRISB = 0x00; // Set portb as output
    portb = 0xFF; // Comments.
    while(1)
    {
        portb = arra[i];
        delay_ms(500);
        i++;
        if (i == 10)
            i = 0;
    }
}
```

Name of Experiment:- Analog signal input in the micro controller or display ADC value in the virtual terminal.

Objectives:

- ① To design a circuit to display ADC value in the virtual terminal
- ② To learn about the display of ADC value in the virtual terminal.

Theory:

The role of ADC converter is to convert analog voltage values to digital values. The ADT converter is to convert analog voltage values to digital values. The ADT converter converts analog voltage to binary numbers. These binary numbers can be in different lengths - 2, 4, 8, 10 bit. The more bits the binary numbers has, the higher the resolution of the A/D. With two bits, we can only display 4 different options

00	01	10	11
----	----	----	----



We can show the changes from 0 to 5 volt with 4 levels

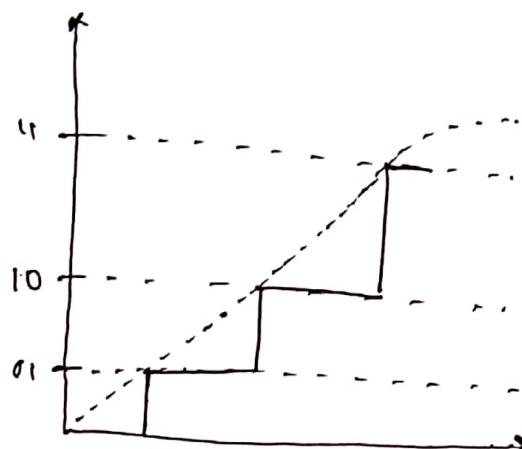


fig: a

We can see from fig-a V_{out} is not close enough to the original analog input voltage values. Thus we can say that A/D with the binary number of two bits has a low resolution and there is a large gap between the real value of the analog value of input voltage and the values represented by the A/D. Now let us consider that the voltage that supplied to the A/D converter is still varies from 0 to 5. Volts, however the A/D converter converts the input voltage to a binary number of three bits, with three bits we can get 8 different options.

000	001	010	011	100	101	110	111
-----	-----	-----	-----	-----	-----	-----	-----

we can see the eight levels in the following illustration

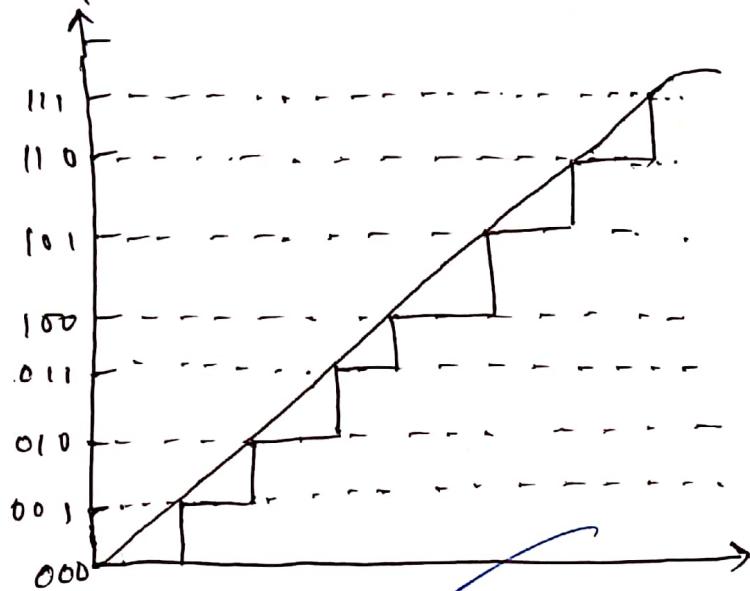


Fig:-b Display eight levels.

from fig-b, we can see that the gap between the analogue signal and the digital is smaller compared to the previous graph.

Therefore we can see that the A/D of the microcontroller with a large amount of bits has a higher resolution A/D takes less time from the conversion time of the high resolution A/D

the ADCON module located within the

PIC microcontroller has a resolution of ten bit length. Therefore, the converter can divide the analog input voltage between 0 to 5V to 2^{10} levels which 1024 levels. we can say that resolution of this component is very high. we can use the triangle method to calculate the binary representation of an analog in voltage.

for example.

let us calculate binary value representation on the analog. input voltage of 3.65 voltage

$$\left. \begin{array}{l} \text{volt} \rightarrow 1024 \\ 3.65V \rightarrow x \end{array} \right\} x = \frac{10240 \times 3.65}{5}$$

≈ 747.522
 $= 748$

Circuit Diagram:-

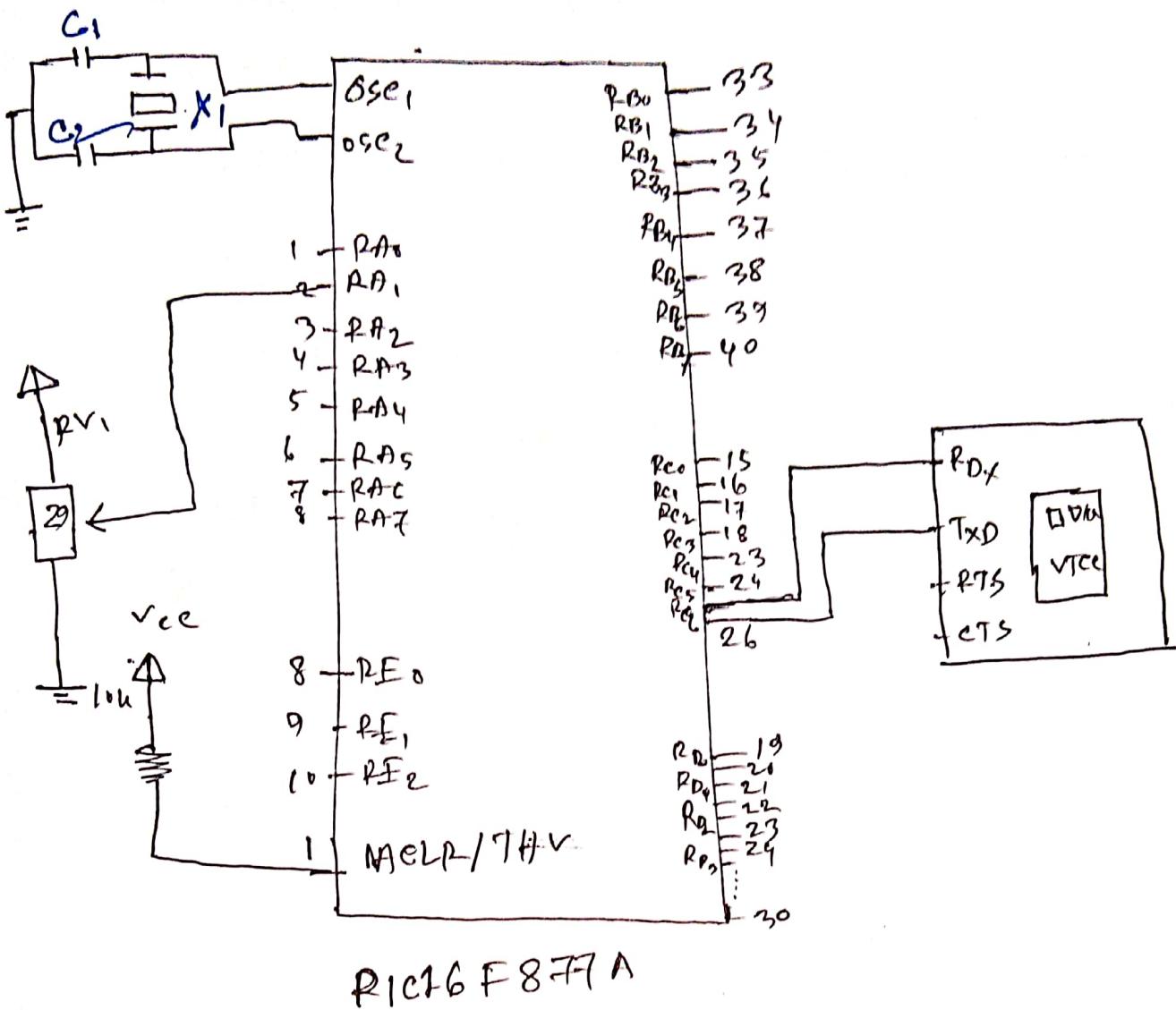


fig :- Displaying ADC value in virtual terminal

'Code!

```
int ValADC;  
char x[4];  
void main()  
{ uAR1, -init (9600);  
    ADC-init();
```

```
while(1){  
    val ADC = ADC - read(0);  
    initstr € ValADC, x);  
    UART1-write-text ("Analog value =");  
    UART1-write-text (n);  
    strcpy (x, " ");  
    UART1-write (13);  
    Delay-ms (1000);  
}  
}
```

one of the experiment: write a program to display 2 digit number using 7 segment multiplexing technique.

Objectives:

- ① Learning how to design a display of 2 digit number using 7 segment multiplexing technique
- ② To learn & understand about multiplexing

Theory:

A seven-segment display is a form of electronic display device for displaying decimal numbers that is an alternative to the more complex dot matrix display.

Multiplexing technique is used for driving multiple seven segment display the theory of 7 segment display is simple all the similar segment of multiple LED display are connected together and driver through single I/O pin






Multiplexing is necessary to interface two or more seven segment display to a microcontroller software program can control these multiplexed seven segment to ON/OFF in a cyclical fashion.

This also helps to reduce power in battery operated systems.


Apparatus Required:-

- ① PIC16F877A, capacitor, resistor, crystal,
- ② button, 2 digit seven segment
- ③
- ④

Circuit Diagram:-

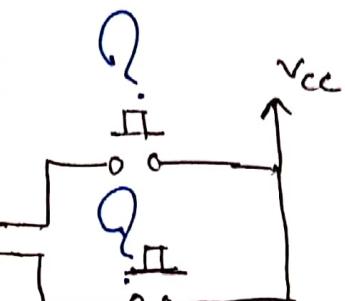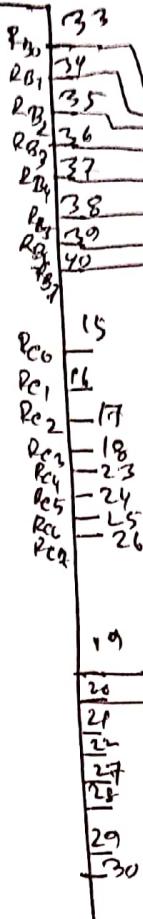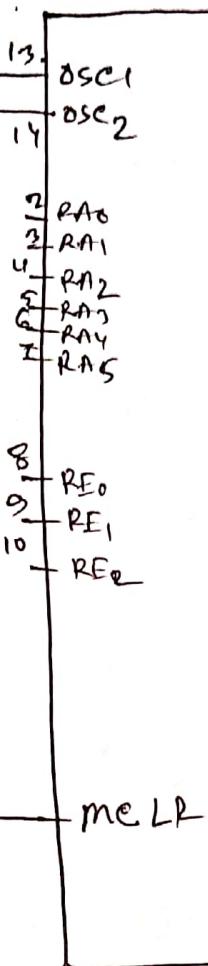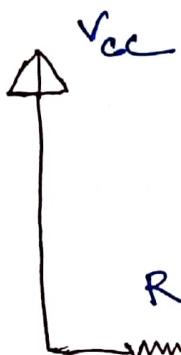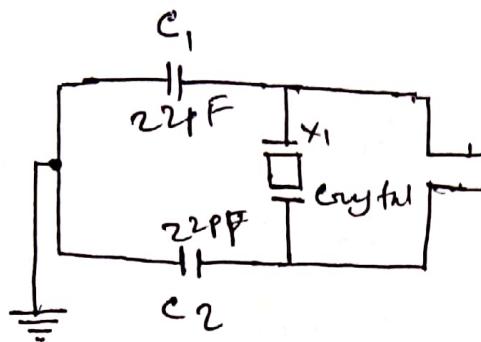

2 digit 7 segment

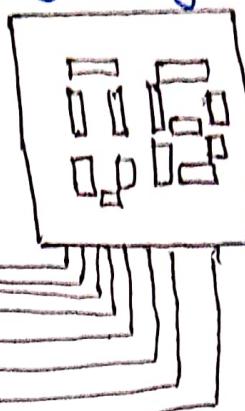

Micro-code:

Char segment [] = { 0x3F, 0x06, 0x5B,

0x4F }

int i=0;

void main() {

 trisb = 0x00;

 trisc = 0x00;

 void main() {

 TRISE = 0x00;

 TRISD = 0x00;

while (1)

```
{ PORTD = 0x80;  
PORTC = 0x00;  
ms_Delay (10)  
PORTD = 0x40;  
PORTE = 0ff;  
ms_Delay (10)  
PORTD = 0x20;  
PORTC = 0xff;  
ms_Delay (10)  
PORTD = 0x10;  
PORTE = 0x10;  
ms_Delay (10);  
  
PORTD = 0x08;  
PORTC = 0x18;  
ms_Delay (10)  
PORTD = 0x02;  
PORTC = 0xff;  
ms_Delay (10);  
  
PORTD = 0x01;  
ms_Delay (10)}
```

}

point b = 0x00;

pointc = 0x00;

trisd = 0x0f

pointd = 0;

while (1)

{ pointc.f0 = 0;

pointb = segment [1%10];

delay - ms(10);

pointc.f0 = 1;

pointb.f1 = 0;

point = segment [1%10];

delay - ms(10);

point.f1 = 1;

if (point.f == 1)

{ i++;

while (pointd.f0 == 1);

if (point.f1 == 1) { i--; while (point.f1 == 1)

{ if (i < 0 || i > 09)

i = 0;

}

Name of the Experiment :- Write a program to interface L_{ED} display with push button using pic microcontroller

Objectives:

- ① To learn push button interfacing with pic micro controller
- ② To learn how to control a led using a push button
- ③ To design and understand the circuit diagram.

Theory:

The push-button is a basic input device in the embedded system. It is used to control the operation of any output device using the microcontroller or control unit.

If basically breaks the electrical circuit and interrupts the flow of current.

The push-button is basic mechanical on-off button that act on control

devices. It short circuit the line when it pressed and opens when it is not pressed.

In circuit pull-up and pull-down used to convert infinite or zero resistance into the digital signal. On the basis of the pull-up and pull-down resistor, we can interface the switch in two ways. The value of pull-up and pull-down resistor depends on the microcontroller.

positive logic:- In this connection, we use a pull-down resistor connected to the ground, when we pressed the switch then logic asserts high and when we disconnect the switch logic assert logic.

Negative logic: ✓

In this connection, we use a pull-up connected to Vcc when we pressed the switch then logic assert high.

Apparatus required: pic16F877A, crystal, capacitor, resistor LED

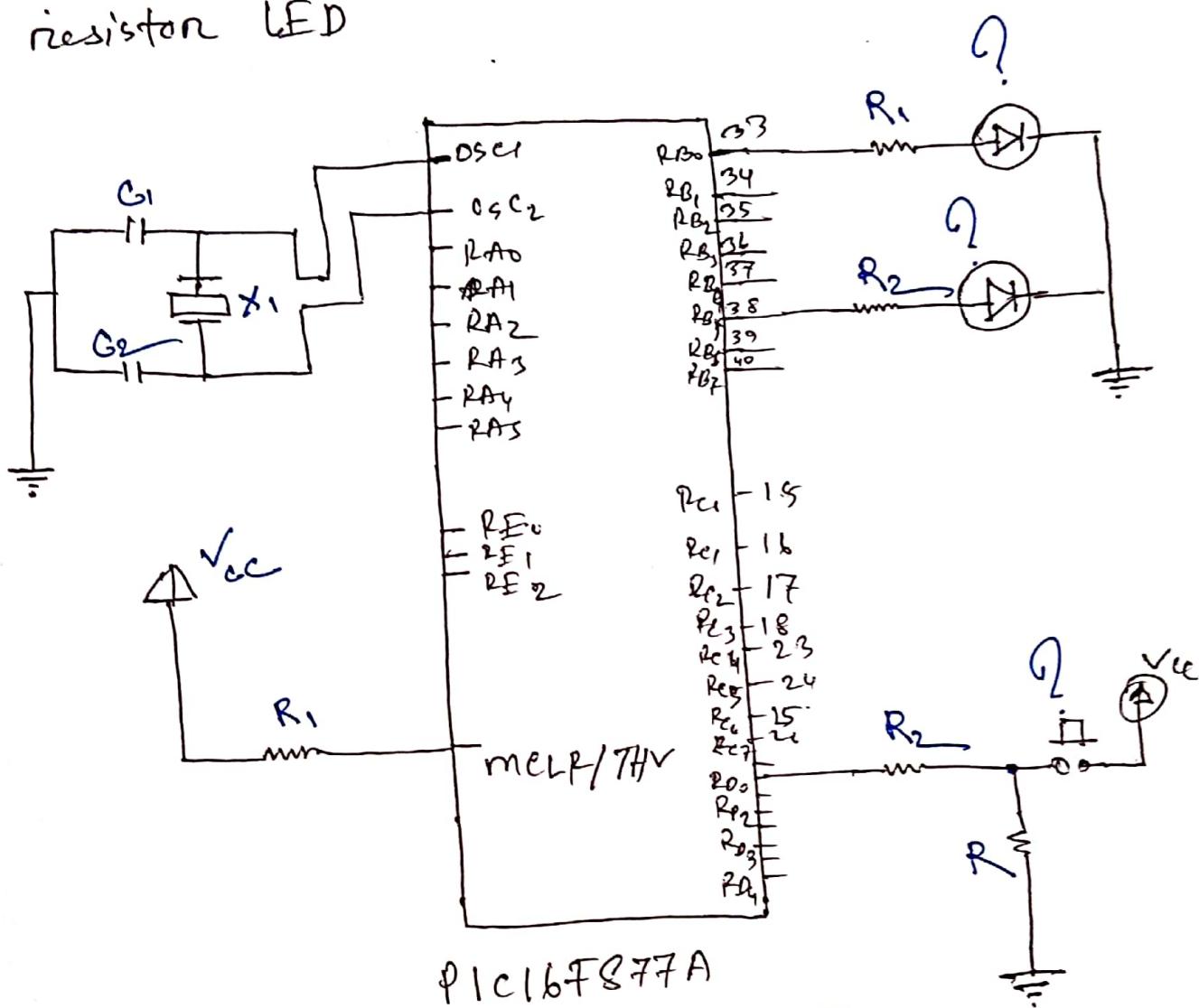


fig: Button interfacing vsig. pic microcontroller

Mikro C program:

```
void main()
{
    int count = 0;
    TRISD = 0xFF;
    TRISB = 0x00;
```

pontb .fo = 0;

while (1)

{ if (pontd .fo == 1)

 delay - ms (200)

 else

 count = 1;

}

 if (count == 0)

 pontb .fo = 0;

 pontb .fs = 0;

 delay - ms (200)

}

 else

 pontb .fo = 1;


 pontb .fs = 1;

 delay - ms (200);

}

}

}

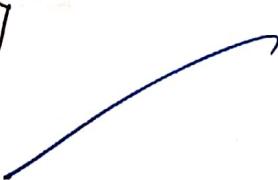

Name of the experiment:- Dot matrix display interfacing with pic16F877A microcontroller

Objects:

- ① To learn Dot matrix display interfacing with pic16F877A microcontroller
- ② To learn how to control Dot matrix display

Theory: A Dot matrix display is a device which contains contains light emitting diodes aligned in the form of matrix. Dot matrix display are used in ~~application~~ where symbol, graphic characters, alphabets number are needed to be displayed in static as well as following motion. A typical dot matrix is shown below:-


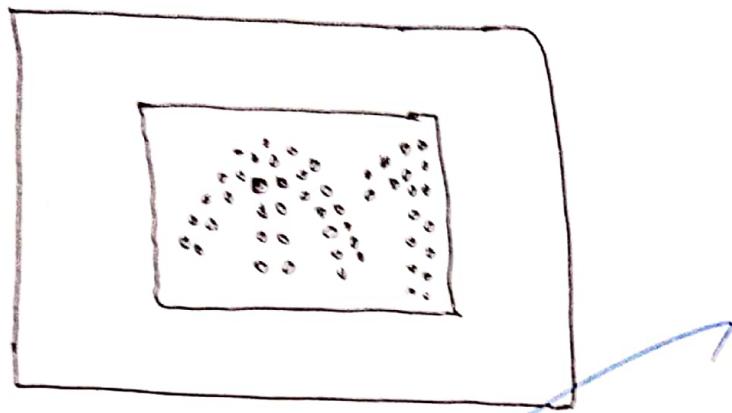


fig:- a typical dot matrix display
is using in lift

Types of dot matrix:

Dot matrix display is manufactured in various dimensions like 5×7 , 8×8 , 16×8 , 32×8 , 64×64 and 128×64 where the numbers represents LED's in rows and columns.

Circuit diagram:

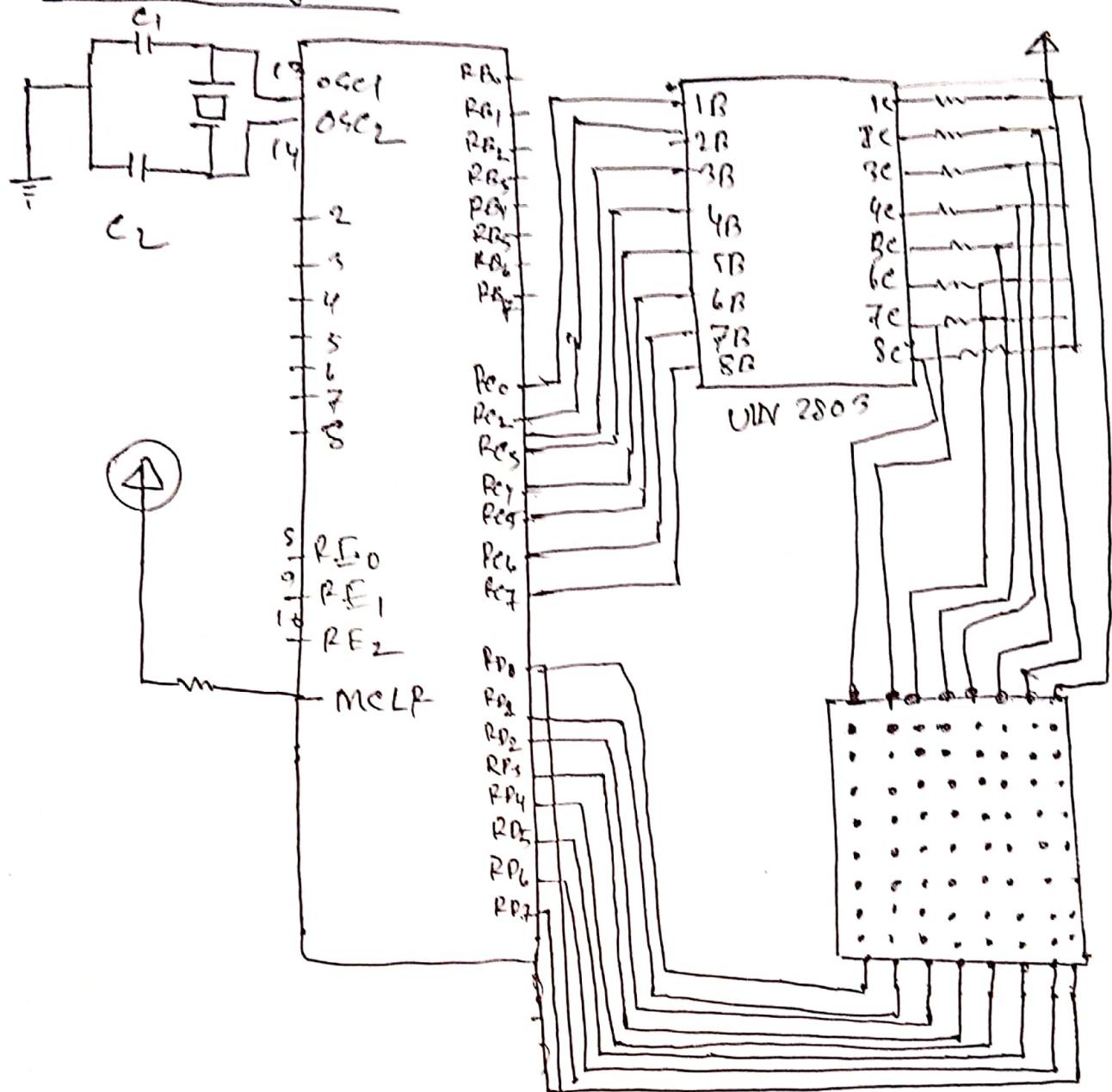

Caption?

Micro C code:

void ms_delay (unsigned char time)

```
    unsigned char y, x;  
    for (y=0; y<time; y++)  
    { for (x=0; x<20; x++);  
    }
```

Experiment no: 4

Experiment name:- LM35 Temperature sensor

Data read and display using LCD

Objectives:

- ① To learn about using LCD module
- ② To learn and understand the circuit diagram of LCD module.
- ③ To learn interfacing LCD with microcontroller

Theory:

To interface LCD with pic microcontroller, we use general purpose input-output pins (GPIO pins). Because we send control and data signal to LCD through these I/O pins.

16x2 LCD pinout:


it consist of 14 pins.

There are 8 data pins from D₀-D₇ and three control pins such as R_S, RW, and E. LED and LED-pins are

LM35 Temperature sensor:-

- LM35 is a temperature measuring device having an analog output voltage proportional to the temperature.
- It provide output voltage in centigrade. It does not require any external calibration circuitry
- The sensitivity of LM35 is $10 \text{ mV}/\text{degree celcius}$. As temperature output voltage also increases.
- It is a 3-terminal sensor used to measure surrounding temperature ranging from -55°C to 150°C
- LM35 gives temperature output which is more precise than resistor output

Circuit Diagram:

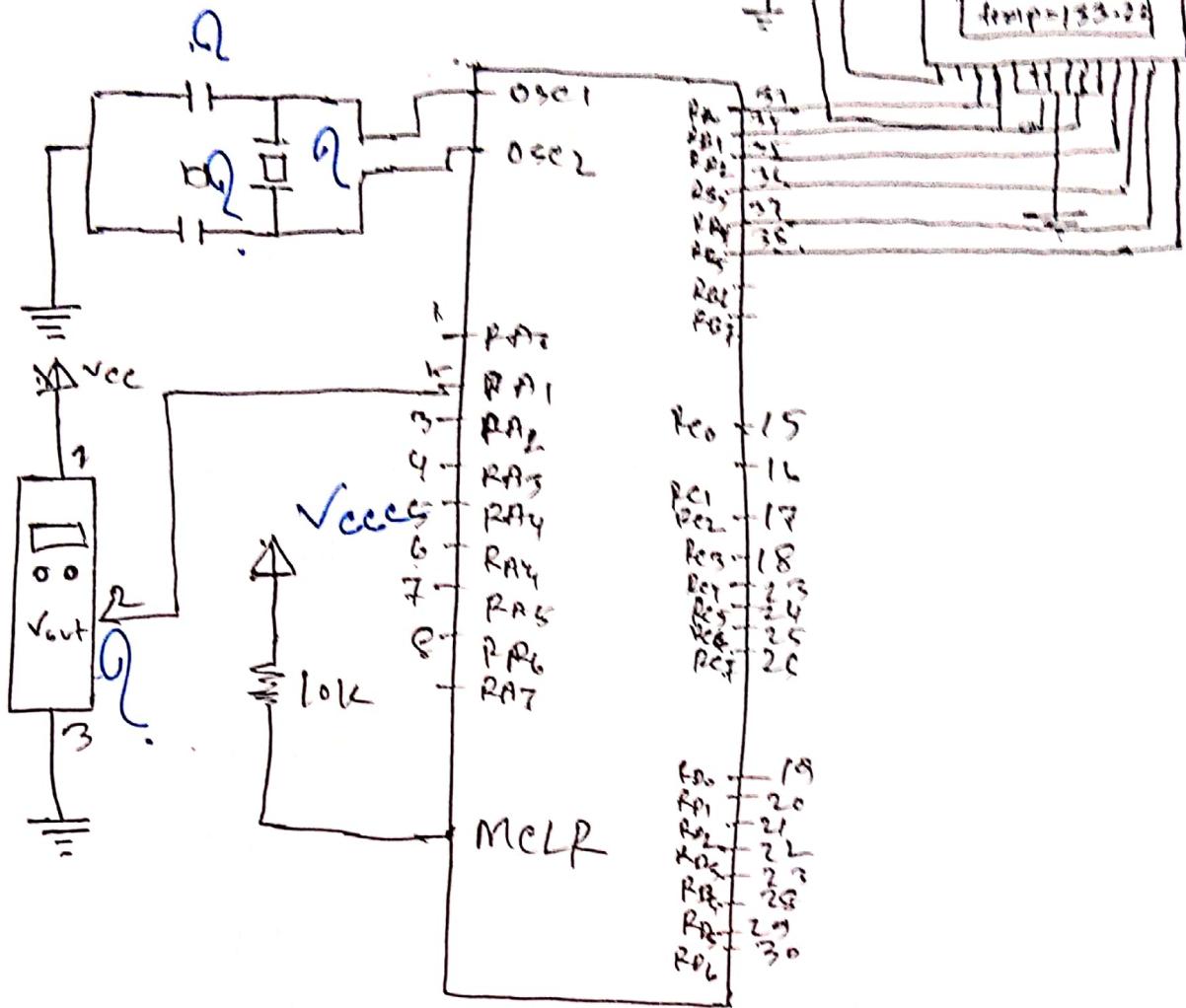

Caption?

Micro - code:

9bit LCD-RS at 230-bit:

shift LCO-EN at R_B , -bit;

shift LCO-DY at EB₂-4F;

9bit LCD - PS and RB₃ - 5f;

shift LCD-D₄ at RBy-bit

shift LCD-D7 at RBS-bit;

9bit LCD_RS_Direction at TRISB1=bit;

shift LCD-EN-Direction at TRISB2-bit)

```
bit LED-05-direction at TRISB5-bit;
bit LED-06-direction at TRISB6-bit;
bit LED-07-direction at TRISB7-bit;
char display[16] = " ";
void main() {
    unsigned int result;
    float volt;
    trisL = 0x00;
    trisA = 0xFF;
    adcon1 = 0x00;
    led-int();
    led-end (-led-clear);
    led-end (-led-cuson-off);
    while(1) {
        result.adc-read(0);
        volt = result * 4.88;
        temp = volt/11;
        led-out(1, "temp:");
    }
}
```

```
sbit LCD-D5 - direction at TRISB5-bit;  
sbit LED-06 - direction at TRISB6-bit;  
sbit LCD-07 - direction at TRISB5-bit;  
char display [16] = " ";  
void main() {  
    unsigned int result;  
    float volt, temp;  
    trisb = 0x00;  
    trisa = 0xFF;  
    adcon1 = 0x80;  
    led-int();  
    led-emd (-led-clear);  
    led-emd (-led-cursor-off);  
    while(1) {  
        result.adc-read (0);  
        volt = result * 4.08;  
        temp = volt / 10;  
        led-out (1, 1, "temp: ");  
    }  
}
```

Experiment no:8

Experiment name: write a program to control a high voltage load using mechanical relay

Objectives:

- ① To learn how to interface ac load through relay with pic microcontroller
- ② To design and operate the circuit of relay interfacing

Theory: A relay is an electromagnetic switch used to switch high voltage current using low power circuits. Relay isolates low power circuits from high power circuit. If it is activated by energizing a coil wounded on a soft iron core. A relay should not be directly connected to a microcontroller.




Because,

- ① A microcontroller is not stable to supply current required for the working of relay. Maximum current that a pic micro-controller handle is 0.5 mA while a relay needs about 50-100mA current
- ② A relay is activated by energizing its coil. microcontroller may stop working by the negative voltage produced in the relay due to its back end.

Apparatus required:

pic16F877A, crystal, capacitor, resistor, transistor, diode, bulb, relay, ac voltage.

Circuit Diagram:

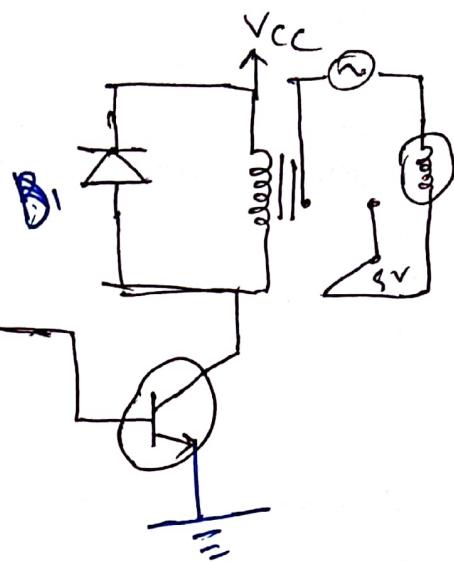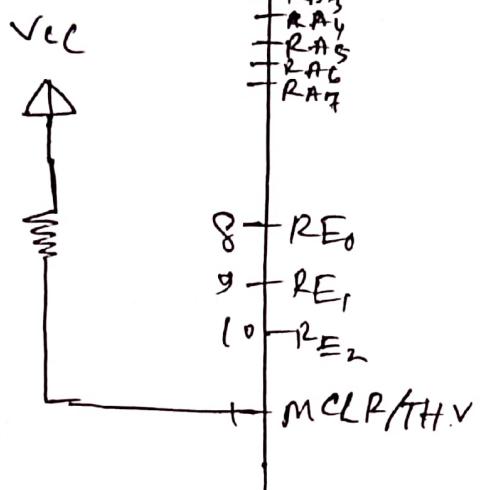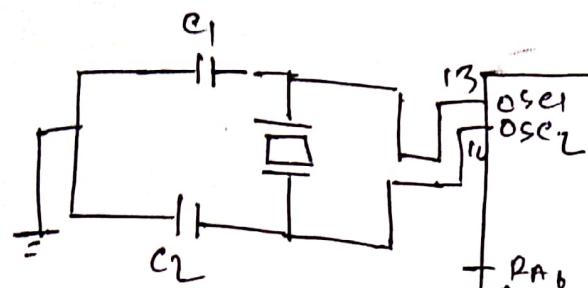

Micro C Code:

```
void main()
```

```
{ TRISB = 0x80;
    portb = 0x01;
```

```
while (1)
```

```
{ portb[1] = 1;
    delay_ms(2000);
    port.b1 = 0;
    delay_ms(200);
```

```
}
```

Experiment no:- 9

Experiment name: DC motor speed control using
pwm power and microcontroller

Objectives:-

- ① To learn how to control the average power delivered to a load using power and how to control the speed of the DC motor
- ② To understand the circuit diagram

Theory: pwm stands for pulse width modulation. A modulation technique that generates variable width pulse to the represent the amplitude of an analog input signal.


pwm is a type of signal which can be produced from a digital IC such as microcontroller or 555 timer. The signal thus produced will have a train of pulses and these pulses will be in form of a square wave. That is, at any given instance of time the wave will either

be high or will be low. The duration at which the signal stays high is called "on time" and the duration at which the signal stays low is called "off time".

Duty cycle of the PWM: A PWM signal stays on for a particular time and stays off for the rest of period. The percentage of time in which the PWM signal remains high is called as duty cycle. If the signal is always on. It is in 100% duty cycle and if it is always off then 0% duty cycle.

formula:
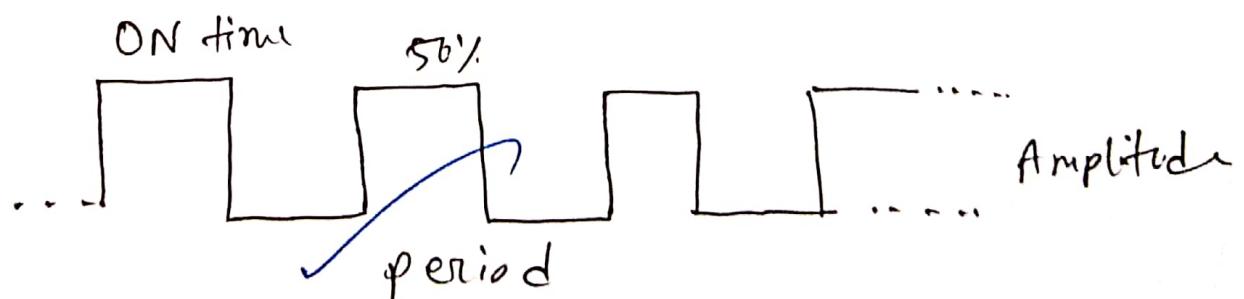
$$\text{Duty cycle} = \frac{\text{Turn ON time}}{\text{Turn on time} + \text{Turn off time}}$$



By controlling the duty cycle from 0


100% we can control the "on time" of pwm signal and thus the width of signal

frequency of pwm :-


$$\text{frequency} = 1 / \text{time period}$$

$$\text{time period} = \text{ON time} + \text{off time}.$$

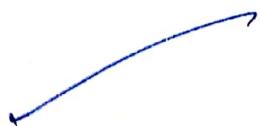Apparatus required:- pic microcontroller, crystal, resistor, capacitor, 2930 IC, DC motor, switch.



Circuit diagram:

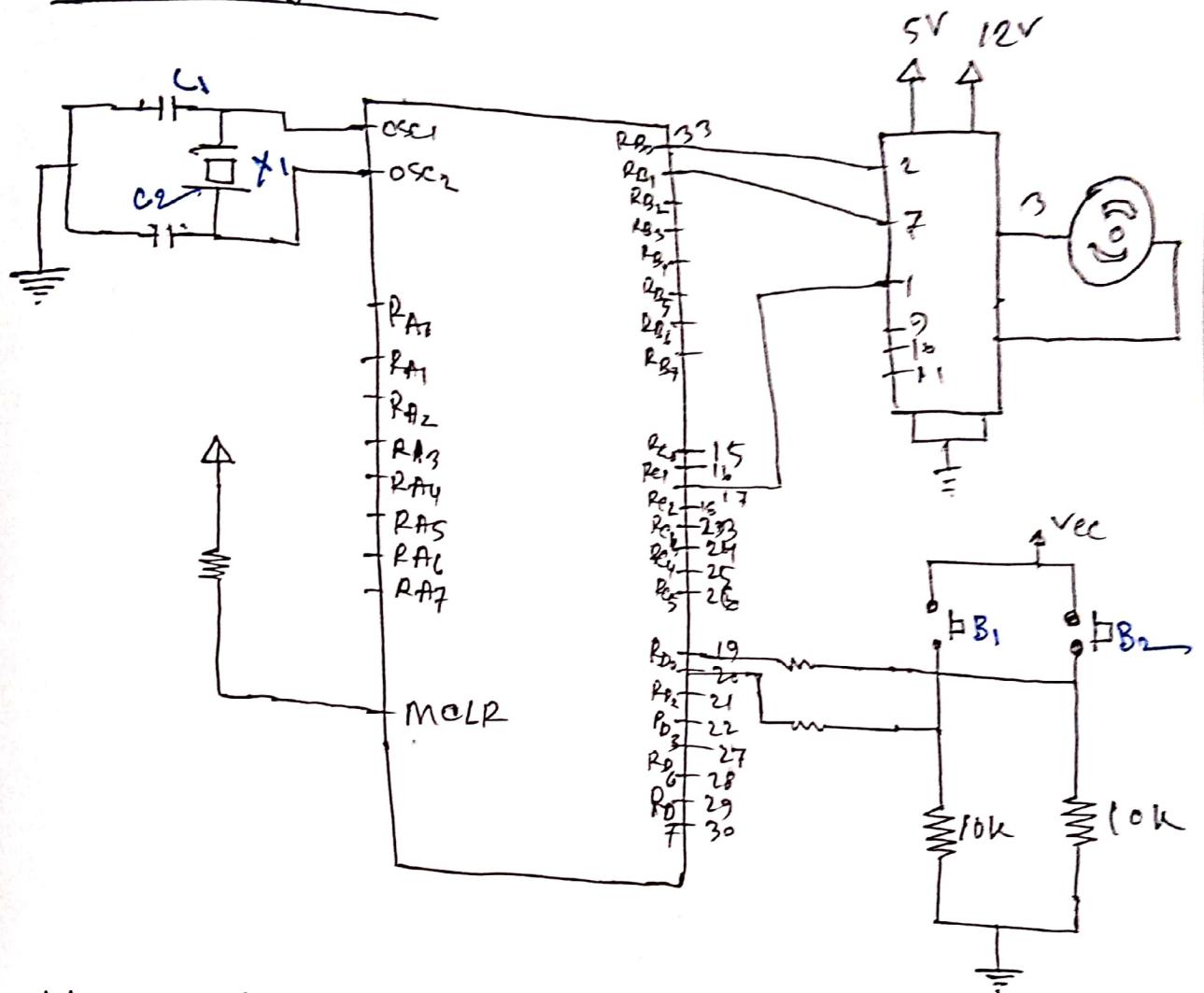

Microcode:

```
void main() {  
    short duty = 0;  
    TRISD = 0xFF;  
    TRISB = 0x00;  
    PORTB.F0 = 0xFF;  
    portB.F1 = 0x00;  
    pwm1 = init(1000);  
    pwm2 = set-duty(duty);
```

```
while(1) {  
    if (RD-bit & & duty > 250)  
        { Relay-mv (100);  
            if (RD0-bit & & duty < 250)  
                {  
                    duty = duty + 10;  
                    PWM1-set-duty (duty);  
                }  
        }  
    if (RD1-bit & & duty > 0)  
        {  
            Relay-mv (100);  
            if (RD1-bit & & duty > 0)  
                {  
                    PWM1-set-duty (duty);  
                }  
        }  
}
```

Experiment No-10

Name of Experiment

control servo motor :- Write a program to
using pic microcontroller

Objectives:

- ① To design and understand the circuit of servo motor
- ② To learn how servo motor works and learn the interfacing of a servo motor with pic16F877A microcontroller
- ③ Programming to control servo motor and hardware connections of servo motor with servo motor with pic16F877A microcontroller.

Theory:


A servomotor is a special kind of motor that operates upon the instructions. It provides it angular precision, which means, unlike other electrical motors that keep on rotating until power is applied to them and stops when the

power is switched off, the servo motor rotates only to a certain degree or until it is required to and then the motor stops and waits for the next instruction to carry out further action. Servo motors are controlled with the help of servo-mechanism. Servo motors are used for precise positioning in robotic arms, legs, etc. Hobby servo motors have three wires two of them (RED and Black) are used to give control signals. Servo can be easily controlled using microcontroller using PWM signals on the control wire. Here we using a servo whose angular rotation is limited to a 180° .

The input to its control line determine the position demanded for the output shaft.

Apparatus required: pic16F87FA, crystal, capacitor, resistor, servo motor.

Circuit Diagram:

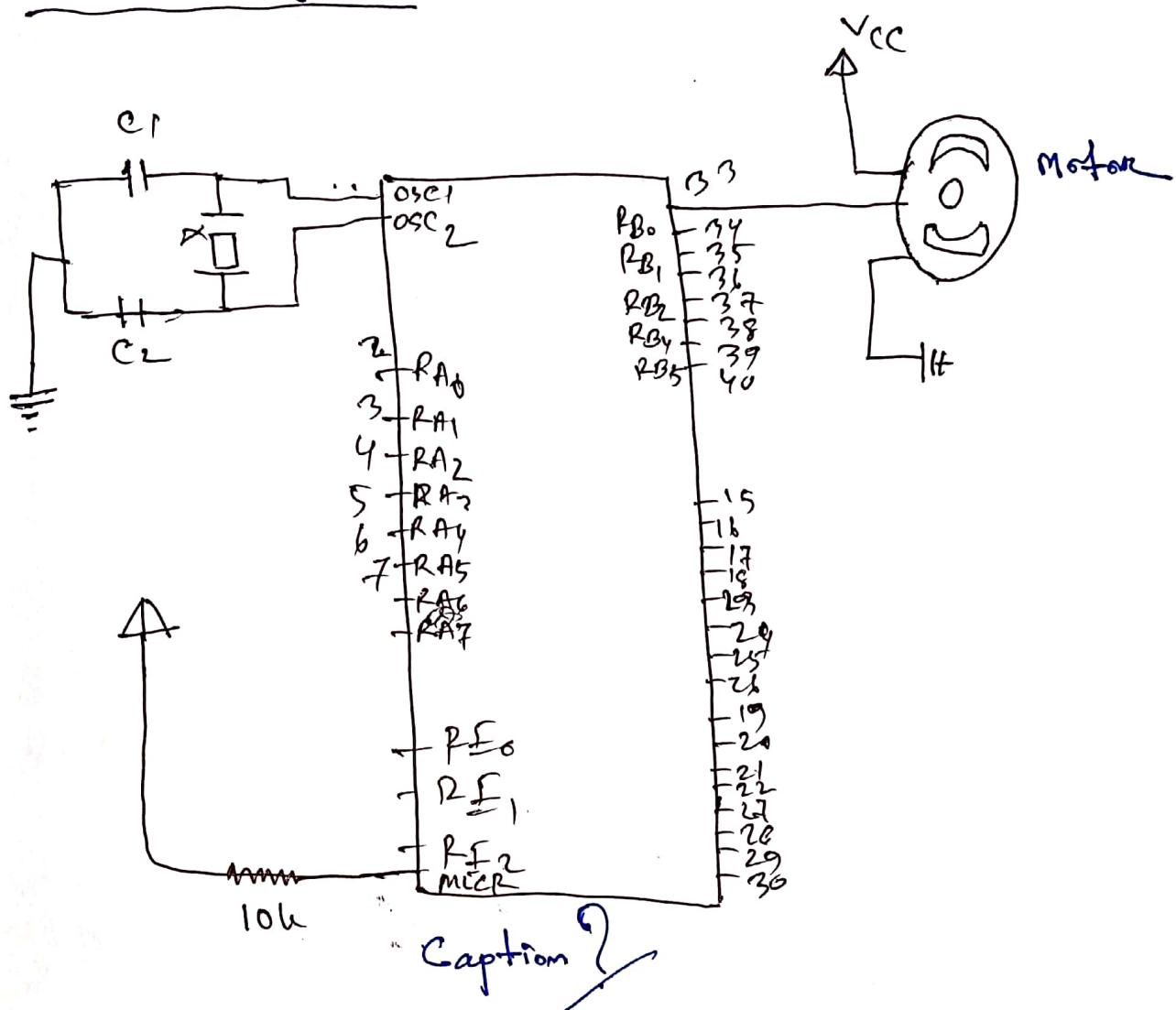

Mikro code:

```
void Servorotate()
{
    unsigned int i;
    for (i=0; i<50; i++)
    {
        portB.F0 = 1;
        delay_us(800);
        portB.F0 = 0;
    }
}
```

```
delay_us(9200);  
}  
void servorotate_90()  
{  
    unsigned int i;  
    for(i=0; i<50; i++)  
    {  
        portB.F0 = 1;  
        delay_us(1500);  
        portB.F0 = 0;  
        delay_us(18500);  
    }  
}  
void servorotate180()  
{  
    unsigned int i;  
    for(i=0; i<50; i++)  
    {  
        portB.F0 = 1;  
        delay_us(2200);  
        portB.F0 = 0;  
        delay_us(1780);  
    }  
}
```

```
void main()
{
    TRISB = 0;
    do {
        servo Rotate();
        Delay_ms(2000);
        Servo Rotate 90();
        Delay_ms(2000);
        servo Rotate 180();
    } while(1);
    while(1)
}
```

Experiment no:- 11

Name of the experiment: write a program for interfacing Stepper motor with pic microcontroller.

Objectives:-

- 1) To describe and explain the operation of a stepper motor.
- ② To design a stepper motor with PIC16F887A and understand its circuit diagram.

Theory: A stepper motor is a brushless, synchronous DC electric motor, which divides the rotation into a number of equal steps. It finds great application in field of microcontroller such as robotics. Unipolar motor is the most popular stepper motor among electronics hobbyist because of its ease of operation and availability.

stepper motor can be easily interfaced with
pic microcontroller by using ready made
ics such as L293D or ULN2003.

We have three different types of stepping
mode for unipolar Stepper motor.

wave drive: In this mode only one stator
electromagnet is energised at a time. It has
the same number of steps as the full step
drive but the torque is significantly less.
It is rarely used. It can be used
where power consumption is more important
than torque.

Wave drive stepping sequence:

Step	A	B	C	D
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1



full drive: In this mode, two stator electromagnets energized at a time.

It is the usual method used for driving and the motor will run at its full torque. in this mode of driving.


full drive stepping sequence:

Step	A	B	C	D
1	1	1	0	0
2	0	1	1	0
3	0	0	1	1
4	1	0	0	1

Apparatus requirement:-

pic16f877A, crystal, capacitor, resistor, steppn,motor, Battany, L293D.

Circuit Diagnosis

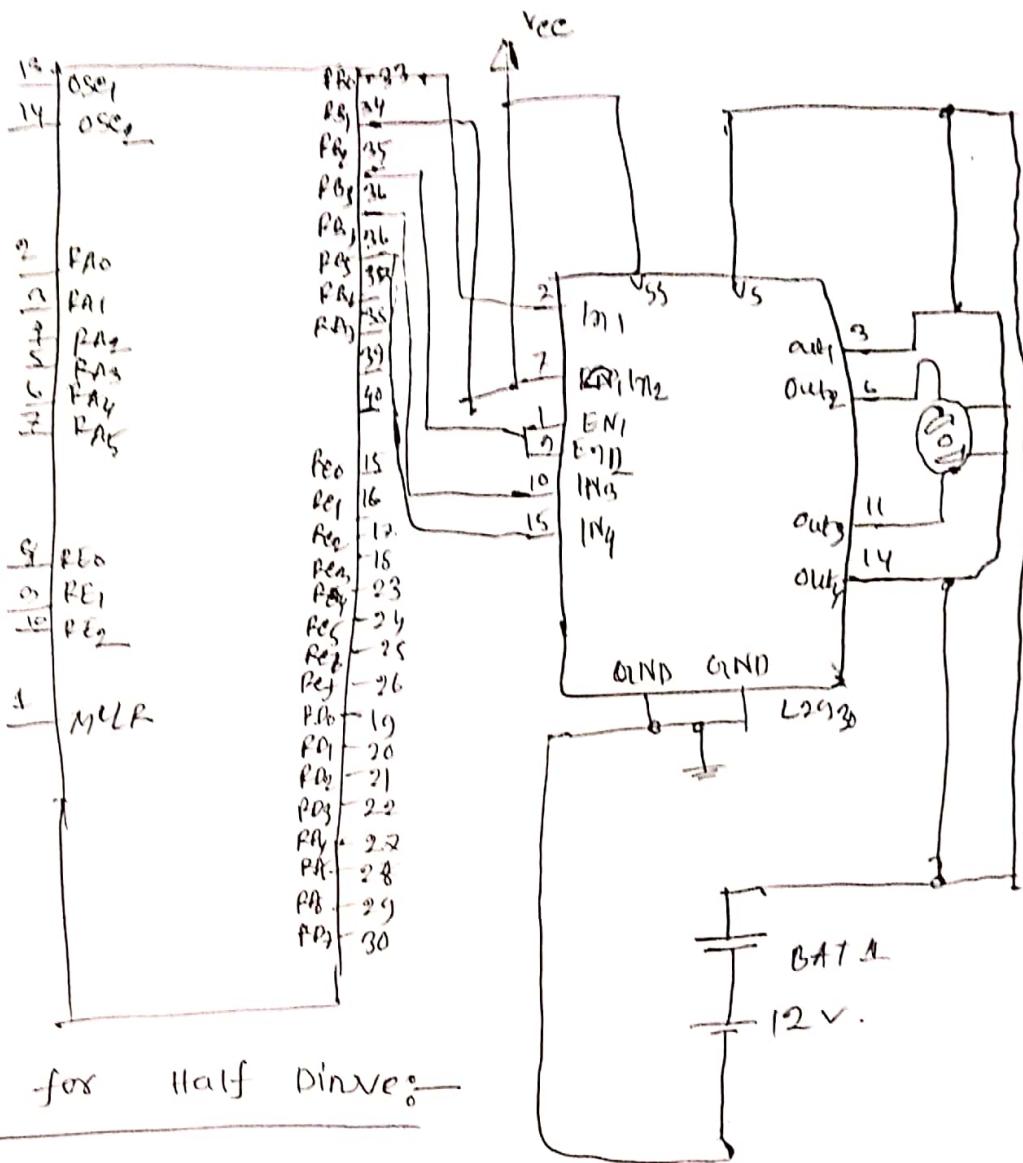

Mikro C code for Half Buses

```
void main()
{
    EMCON = 0x07;
    ADCON1 = 0x06;
    TRISB = 0;
    PORTB = 0xF;
    do {
        PORTB = 0b00000001;
        relay_ms(500);
    } while (1);
}
```

PORTB = 0b0000 0011;

delay-ms(500)

PORTB = 0b0000 0010;

delay-ms(500)

PORTB = 0b0000 100

delay-ms(500)

PORTB = 0b0000 1100;

delay-ms(500);

PORTB = 0b0000 1000;

delay-ms(500);

PORTB = 0b0000 1001;

delay-ms(500);

} while(1);

}.